 


## 3.6 Sequential Circuits

- Combinational logic circuits are perfect for situations when we require the immediate application of a Boolean function to a set of inputs.
- However, when we need a circuit to change its value with consideration to its current state as well as its inputs.
  - These circuits have to “remember” their current state.
- *Sequential logic circuits* provide this functionality for us.


## 3.6 Sequential Circuits

- As the name implies, **sequential logic circuits** require a means by which **events can be sequenced**.
- State changes are controlled by clocks.
  - A “clock” is a special circuit that sends electrical pulses through a circuit.
- Clocks produce electrical waveforms such as the one shown below.



 
## 3.6 Sequential Circuits

- State changes occur in sequential circuits only when the **clock ticks**.
- Circuits can change state on the rising edge, falling edge, or when the clock pulse reaches its highest voltage.




 
## 3.6 Sequential Circuits

- Circuits that change state on the rising edge, or falling edge of the clock pulse are called **edge-triggered**.
- *Level-triggered circuits* change state when the clock voltage reaches its highest or lowest level.



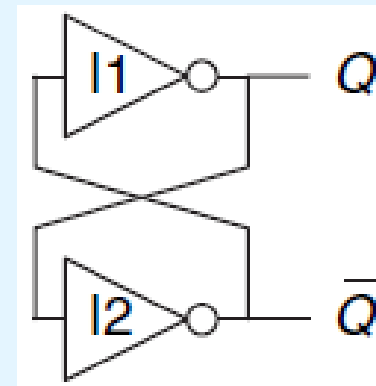 
## 3.6 Sequential Circuits

- To retain their state values, sequential circuits rely on *feedback*.
- **Feedback** in digital circuits occurs when an output is looped back to the input.
- A simple example of this concept is shown below.
  - If  $Q$  is 0 it will always be 0,
  - if it is 1, it will always be 1.
  - Why?



 
## 3.6 Sequential Circuits

- You can see how feedback works by examining the most basic sequential logic components, the **SR Latch**.
  - The “SR” stands for set/reset.
- The internals of an SR latch are shown below, along with its block diagram.


 
# 3.6 Sequential Circuits

- The behavior of an SR flip-flop is described by a characteristic table.
- $Q(t)$  means the value of the output at time  $t$ .  
 $Q(t+1)$  is the value of  $Q$  after the next clock pulse.



S	R	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	undefined

# RS- Latch

 


Figure (a)

Case  $Q=0$

Because  $S$  and  $Q$  are FALSE,  $N2$  produces a TRUE output on  $Q$ , as shown in Figure (a). Now  $N1$  receives one TRUE input,  $Q$ , so its output,  $Q$ , is FALSE, just as we had assumed.

 



Figure (b)

Case  $Q=1$

Because  $Q$  is TRUE,  $N2$  produces a FALSE output on  $Q$ , as shown in Figure (b). Now  $N1$  receives two FALSE inputs,  $R$  and  $Q$ , so its output,  $Q$ , is TRUE, just as we had assumed.


 
When  $R$  and  $S$  are 0,  $Q$  will remember this old value,  $Q(t)$ . **This circuit has memory.**





a) SR-latch

S	R	Present State Q(t)	Next State Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	Undefined
1	1	1	Undefined

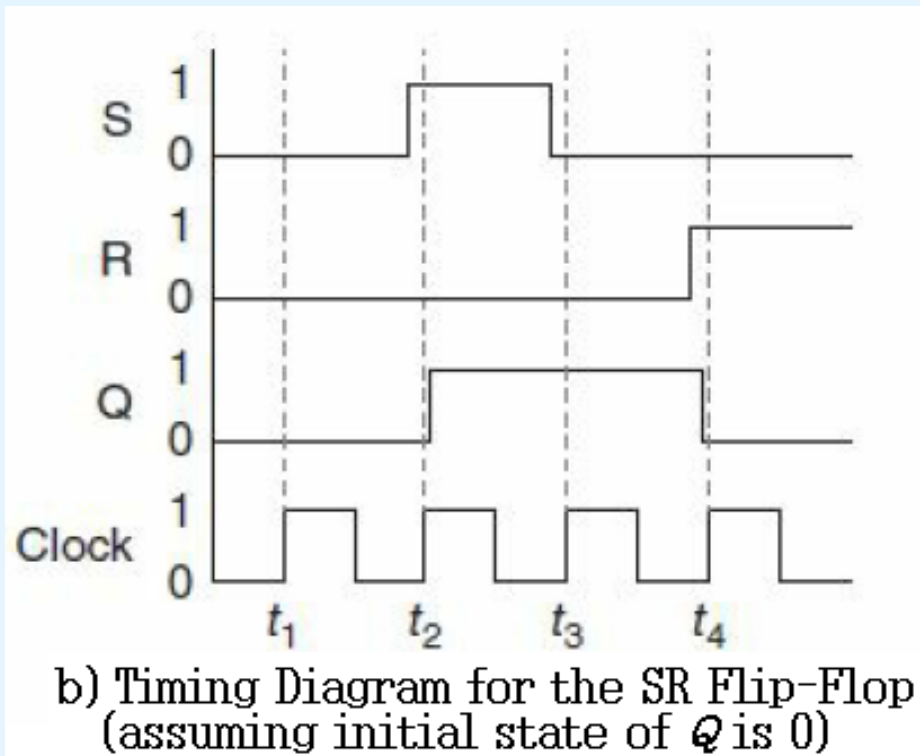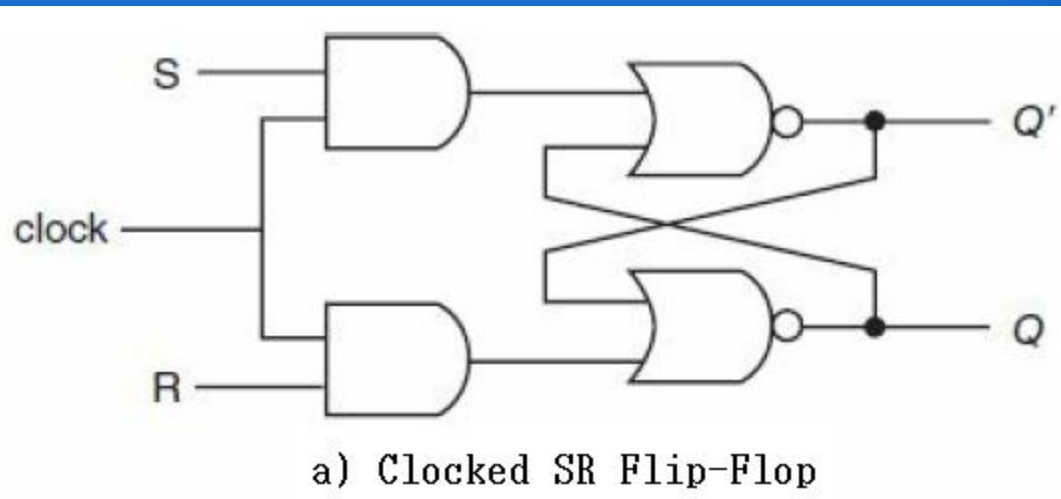


# 3.6 Sequential Circuits

## JK Flip-Flop

- RS Flip-Flop ห้ามไม่ให้ R และ S = 1 พร้อมกัน
- JK Flip-Flop ใช้ได้ทุกเหตุการณ์

J	K	Q
0	0	คงที่ (Latch)
0	1	0
1	0	1
1	1	เปลี่ยนเป็นตรงข้ามกับสถานะเดิม Toggle

 


# 3.6 Sequential Circuits

## JK Flip-Flop ที่มีสัญญาณนาฬิกา

- RS Flip-Flop ห้ามไม่ให้ R และ S = 1 พร้อมกัน
- JK Flip-Flop ใช้ได้ทุกเหตุการณ์


J	K	Q
0	0	คงที่ (Latch)
0	1	0
1	0	1
1	1	เปลี่ยนเป็นตรงข้ามกับสถานะเดิม Toggle

 

clk = 0 ทำให้ Q มีค่าคงสถานะเดิมตลอด

# 3.6 Sequential Circuits


## ตัวอย่างวงจร (ต่อ)

 

- จากวงจรให้พิจารณาว่าเมื่อ Clock ลูกที่ 1, 2, 3, 4 และ 5 กระตุ้น  $Q_1, Q_2$  แต่ละช่วงมีค่าเท่าไร

# 3.6 Sequential Circuits

## D-Latch


 


The data input, ***D***, controls what the next state should be.

The clock input, ***CLK***, controls when the state should change.

<b><i>CLK</i></b>	<b><i>D</i></b>	<b><math>\bar{D}</math></b>	<b><i>S</i></b>	<b><i>R</i></b>	<b><i>Q</i></b>	<b><math>\bar{Q}</math></b>
0	X	$\bar{X}$	0	0	$Q_{prev}$	$\bar{Q}_{prev}$
1	0	1	0	1	0	1
1	1	0	1	0	1	0

# LAB2 Sequential Circuits

 
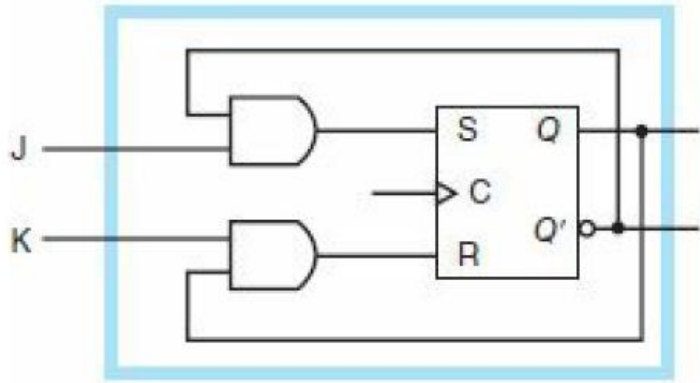


## 1. จากวงจร JK flip-flop

- ให้ต่อวงจรให้สร้าง Truth table และ Timing diagram
- ให้อธิบายการทำงานของวงจรตาม Truth table และ Timing diagram



## 2. จากวงจร D flip-flop ให้ทำตามขั้นตอนของ JK flip-flop

# JK Flip-flop

 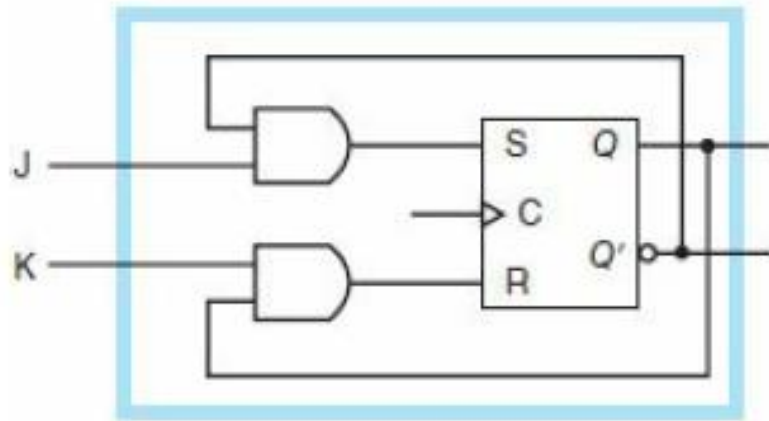



# D Flip-flop

  

# Ex. Sequential Circuits


- Registers,
- counters,
- memories, and
- shift registers

# 3.6 Sequential Circuits


- 4-bit register consisting of four D flip-flops. You will usually see its block diagram (below) instead.



 **A larger memory configuration is shown on the next slide.**



# 3.6 Sequential Circuits

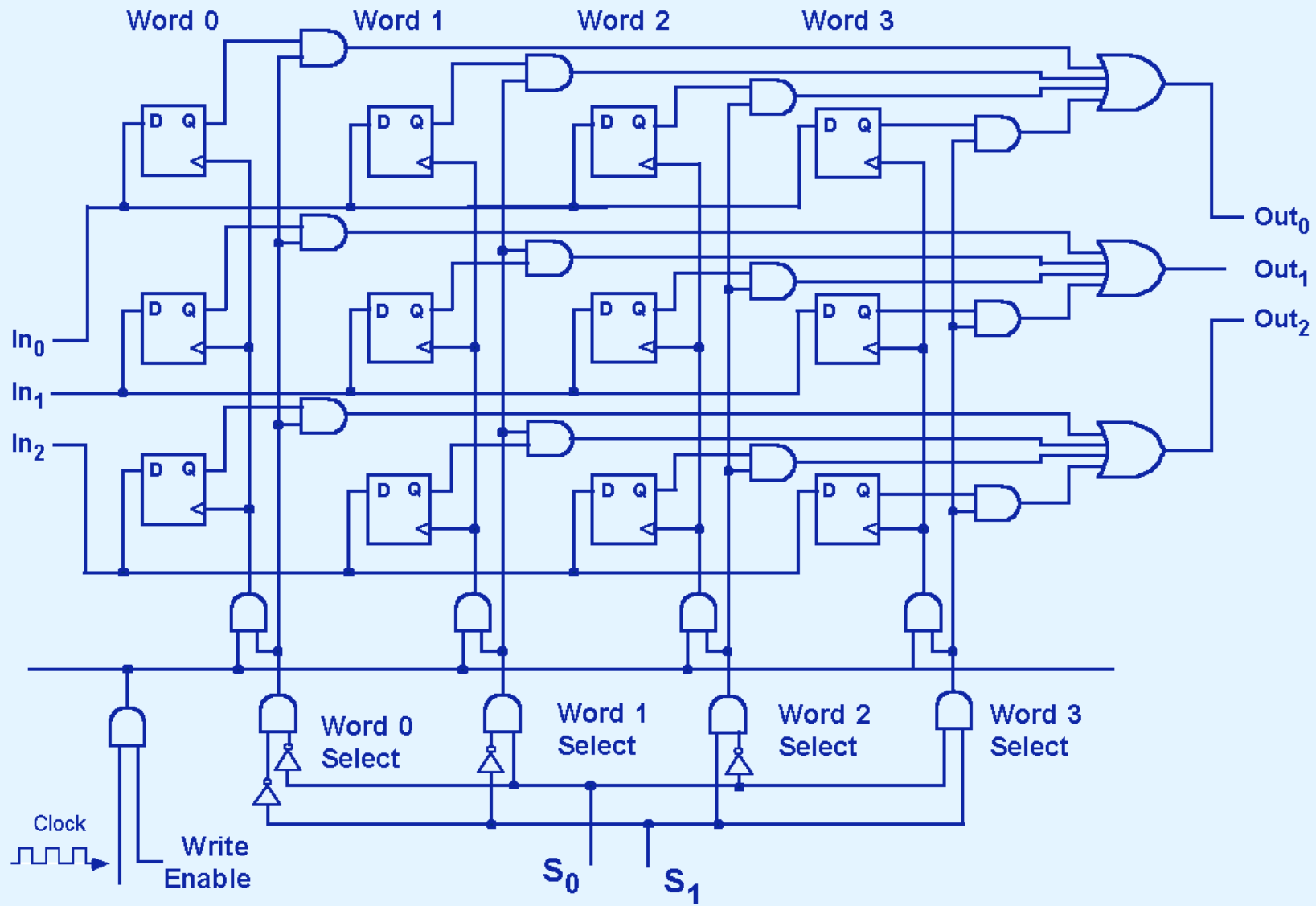

# 3.6 Sequential Circuits

- A binary counter is another example of a sequential circuit.
- The low-order bit is complemented at each clock pulse.
- Whenever it changes from 0 to 1, the next bit is complemented, and so on through the other flip-flops.

